

Preparation


Half-Adder

Logic Diagram



A	B	S	C
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1


Circuit Schematic

 

74HCT86: VCC = P14
GND = P7
74HCT08: VCC = P14
GND = P7


Full-Adder

Logic Diagram

 

A	B	CI	S	C
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1


Circuit Schematic

 

74HCT86: VCC = P14
GND = P7
74HCT08: VCC = P14
GND = P7
74HCT32: VCC = P14
GND = P7


Prep Cont.

Parallel Adder

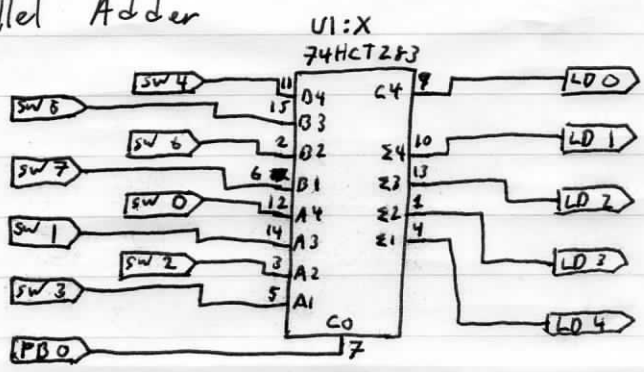

74HCT283:
VCC = P16
GND = P8

Adder - Subtractor

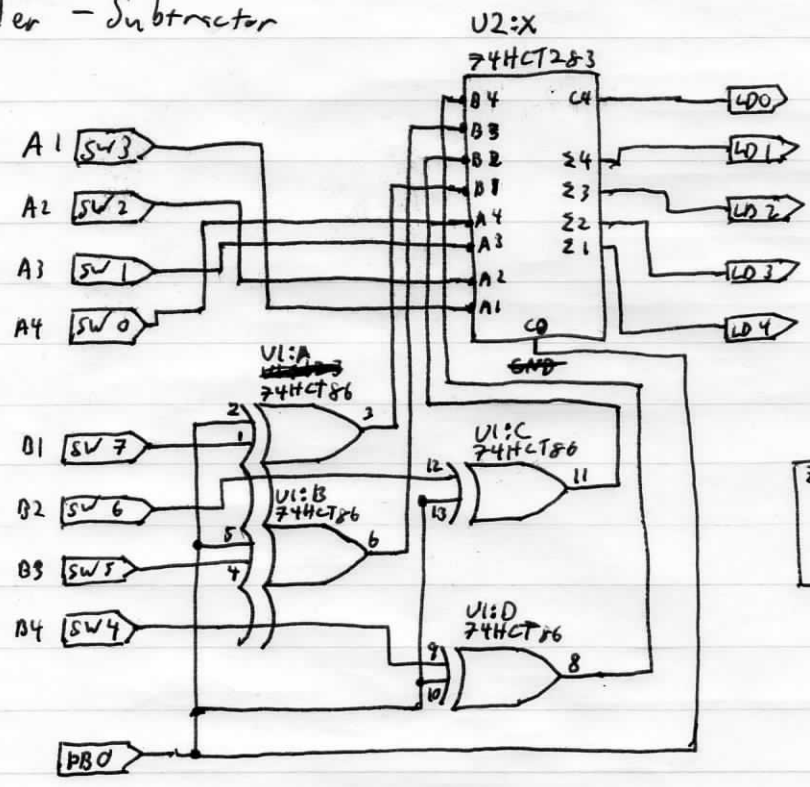

74HCT283:
VCC = P16
GND = P8

Prac 2

Procedure

0) Initialize breadboard with VCC, GND, and wire up to all chips.

1) Construct and test half-adder

A	B	SC
1	1	0 1
1	0	1 0
0	1	1 0
0	0	0 0

Consistent w/ prep

2) Construct full adder - Consistent with Prep and Logisim

3) Construct Adder-Subtractor - Consistent with Logisim

4) Investigate 7-seg display

Each digit in hex has 4 digits in binary

Don't use /LE or /RBI

Conclusion

It is very important to test along the way. Equipment may be faulty so debugging early will catch that early.

The 7-seg display indicates hex digits which must be wired according to the binary LSB and MSB.

To implement subtraction we used XOR gates to take the one's complement of one set of inputs but two's complement must be used to implement subtraction with an adder. We used a Mode Switch to set one's complement when it is 1 so we wired the mode switch to the carry in of the adder which will give two's complement when the mode switch is high.

Tutor Task

A) $12 - 8 = C_x + (-1)8 = 4$, Tested \rightarrow

A	B	S
C	8	4

B) $A_x + 2 = 10 + 2 = 12 = C_x$ Test \rightarrow

A	2	C
---	---	---

C) $6 - 10 = 6 - A_x = -4 = -1(4) = C_x$ Test \rightarrow

6	8	C
---	---	---

D) $2 - (-2) = 0010 - (-1)0010 = 0010 - 1110 = 2 - 14 = 2 - E_x = 0$

Test \rightarrow

2	E	0
---	---	---