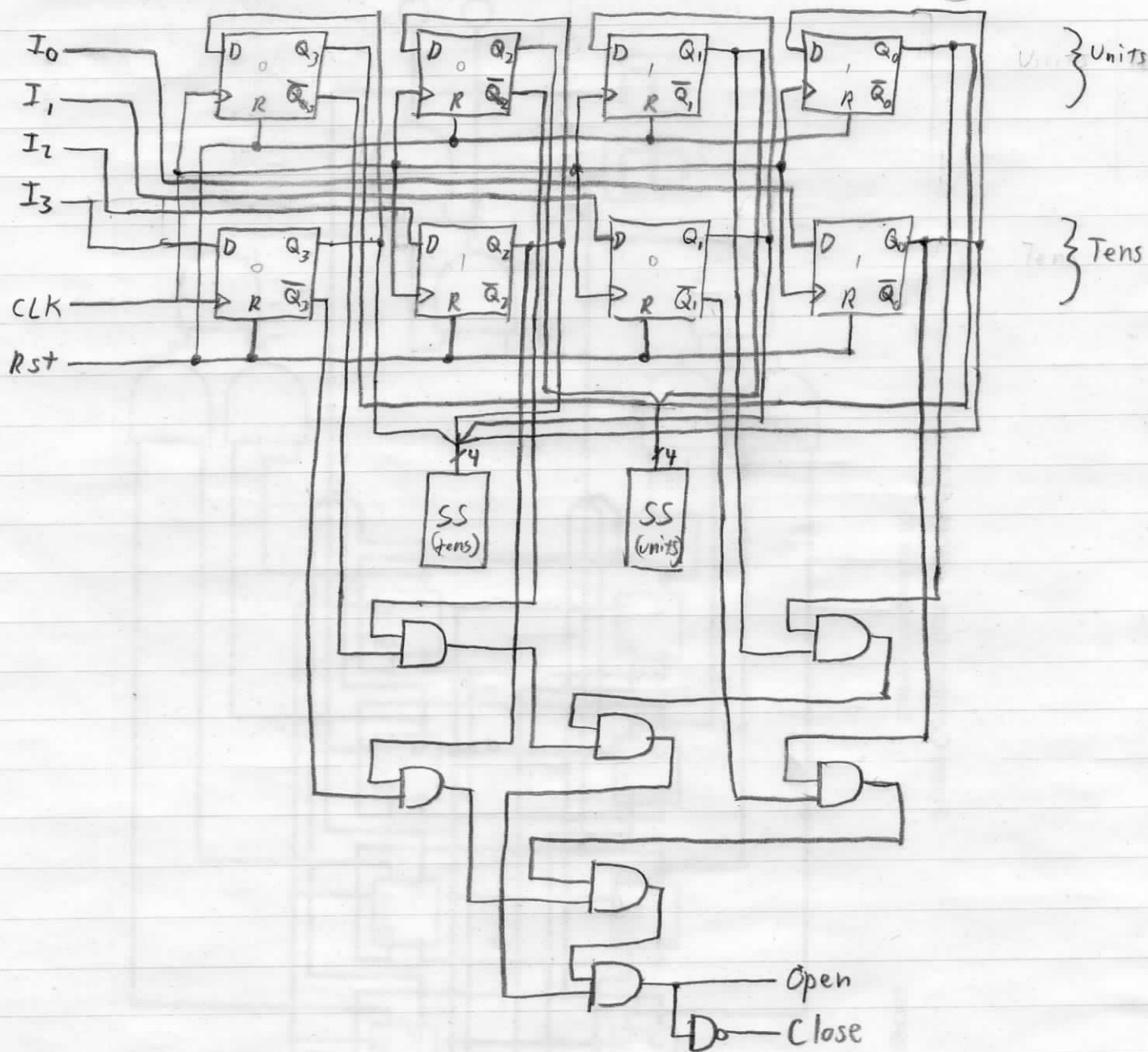


Prac4

42094353

1 prep ng Justin Mancinelli
1 Doc ng
1 Demo ng
4/4 ng


Logic Diagram.



Prac 4

42094353

Circuit Schematic

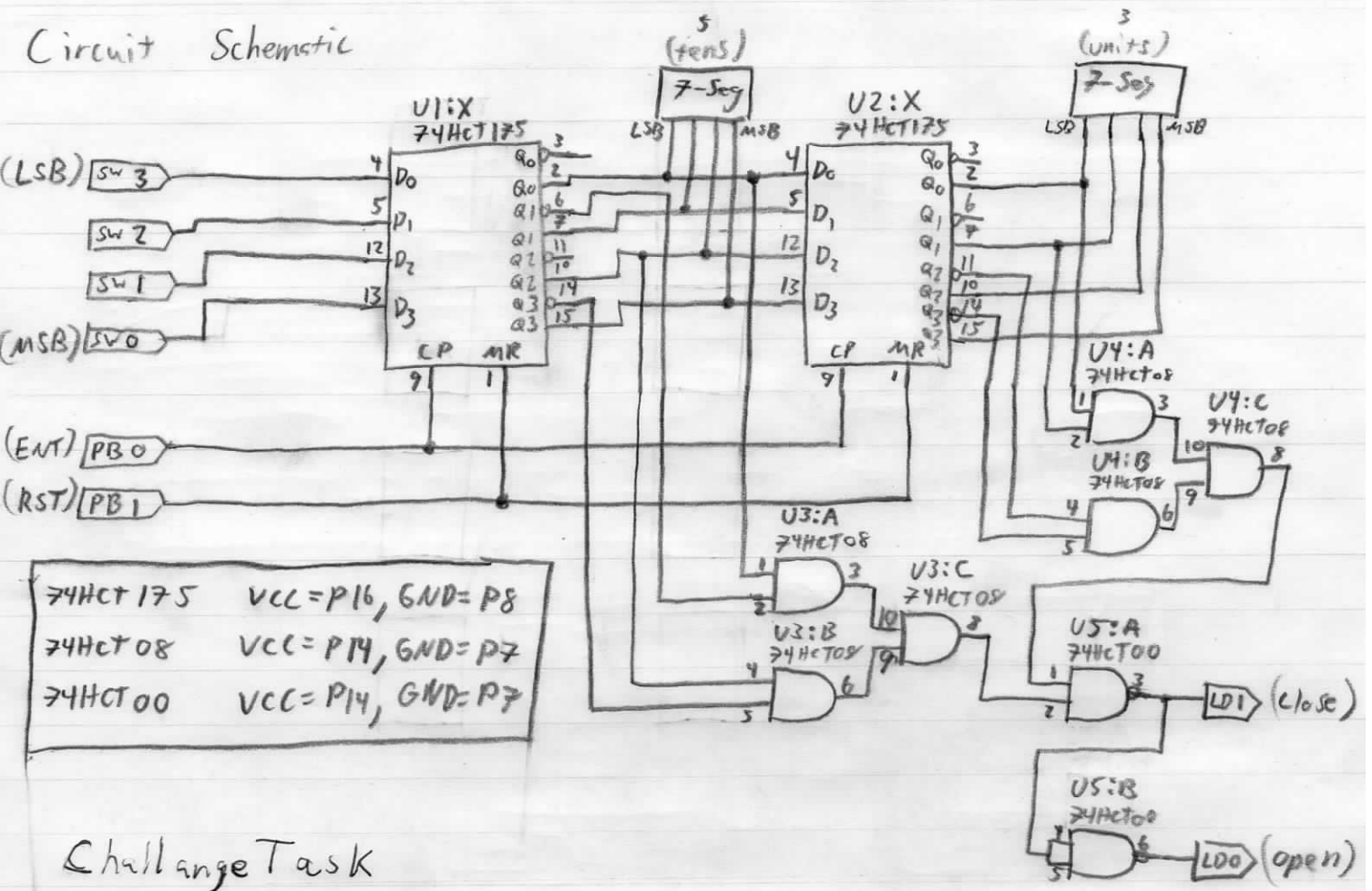


Challenge Task

Programmable Combination Lock MUXs (1 of 1)

Justin Mancinelli 42094353

Correct Combination: 53

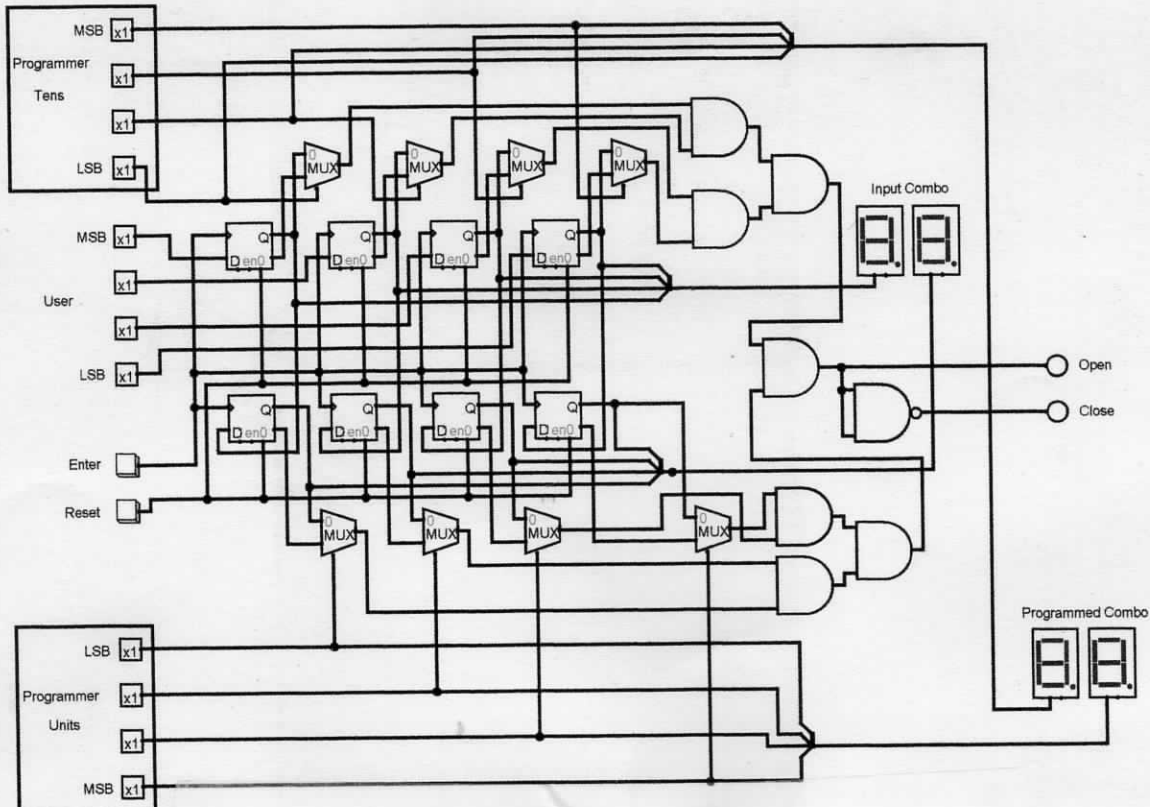


Prac 4

Challenge Task Cont.

Programmable Combination Lock XORs (1 of 1)

Justin Mancinelli 42094353

Correct Combination: 53

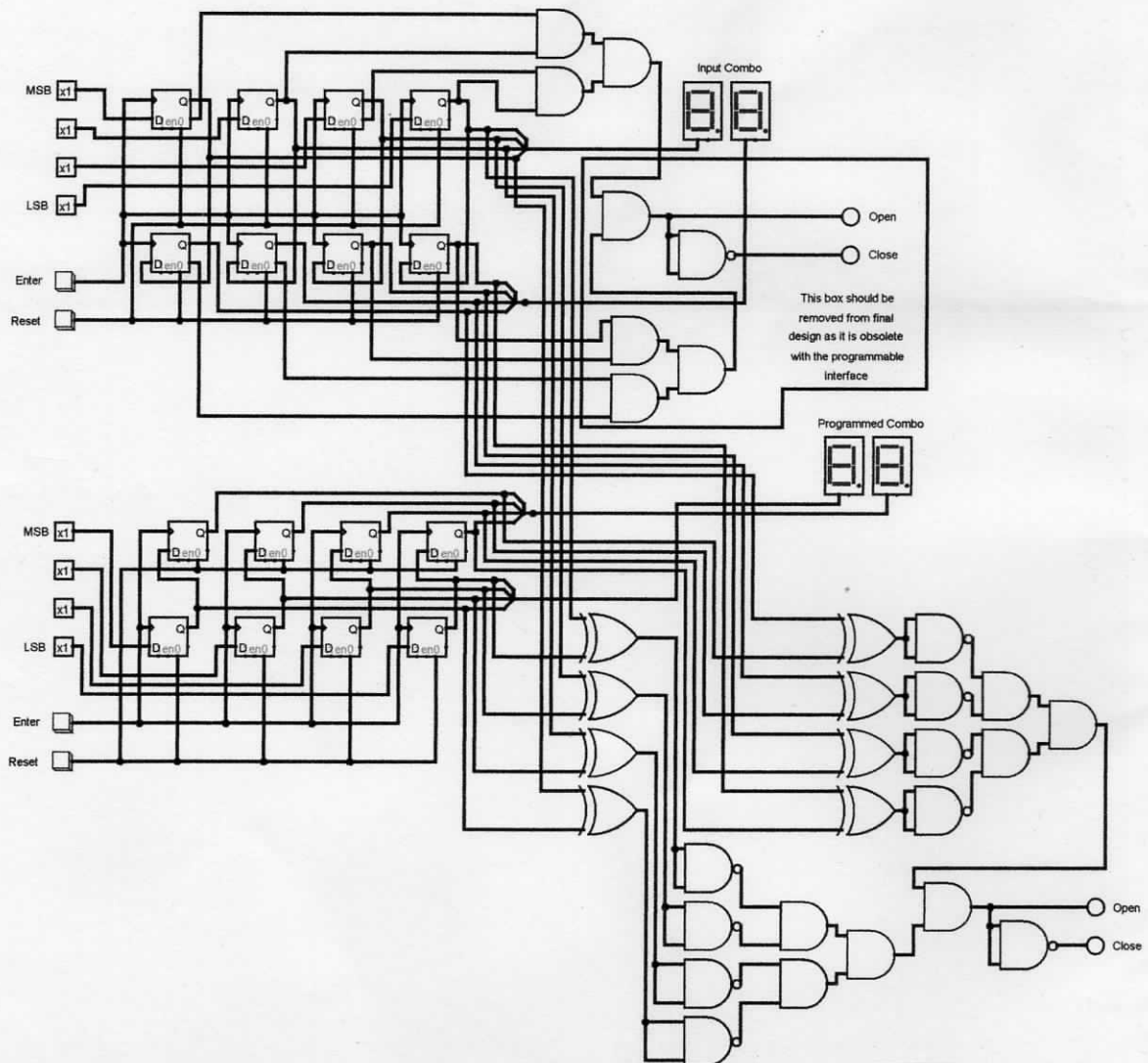

Procedure

- ① Wire SWX and PBX to 74HCT175
- ② Wire both 74HCT175 to each other and the Hex Displays.
- ③ Test using Hex Display — All good
- ④ Hardwire Tens and Units Digits
- ⑤ Test Tens and units individually — All good
- ⑥ Wire Open and Close LEDs to logic.
- ⑦ Test various combinations for LED output — All good

Combination Lock successfully wired for code 53.

Tutor Task: Change Code to 8B

- ① To change the code, note that the Q outputs from the 74HCT175 just need to be rewired to the binary representation.

$$8_{16} = 1000_2 \Rightarrow Q_3 \overline{Q_2} \overline{Q_1} \overline{Q_0} \text{ on U1}$$

$$B_{16} = 1011_2 \Rightarrow Q_3 Q_2 Q_1 Q_0 \text{ on U2}$$

- ② U1: P15, P11, P6, P3
U3: P1, P2, P4, P5

U2: P15, P11, P7, P2

U4: P1, P2, P4, P5

- ③ Rewire as in ② and test individually — All good
- ④ Test various combinations for LED output — All good

Combination Lock successfully rewired for code 8B.